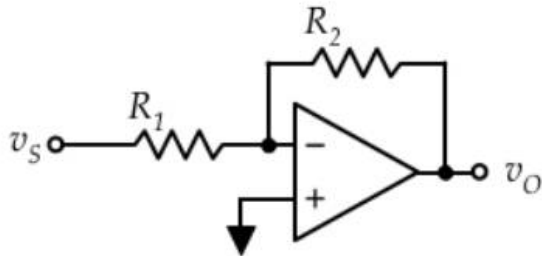


In the circuit shown below $R_2 = 17.5 \text{ k}\Omega$.

Assume that the op-amp is ideal.

Determine the value of R_1 so that the *magnitude* of closed-loop gain, $G = v_O / v_S$ is 7.




[Answer](#)

$$R_1 = 2.5 \text{ k}\Omega$$

In the circuit shown below $R_1 = 10 \text{ k}\Omega$, $R_2 = 8 \text{ k}\Omega$ and $R_3 = 48 \text{ k}\Omega$

Assume that the op-amp is ideal.

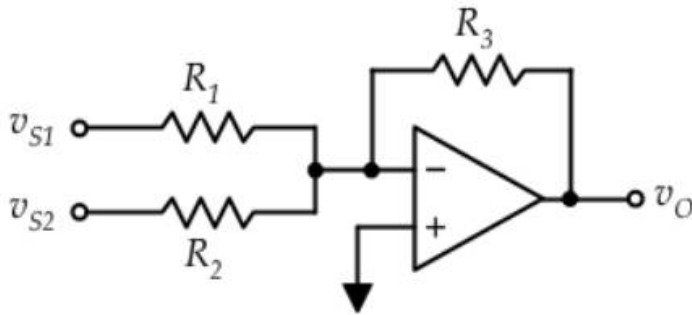If $v_{S1} = 0.8 \text{ V}_{\text{DC}}$ and $v_{S2} = -0.5333 \text{ V}_{\text{DC}}$ determine the DC output voltage.




[Answer](#)

$$v_O = -0.64 \text{ V}_{\text{DC}}$$

In the circuit shown below $R_1 = 6 \text{ k}\Omega$ and $R_2 = 132 \text{ k}\Omega$.

Assume that the op-amp is ideal.

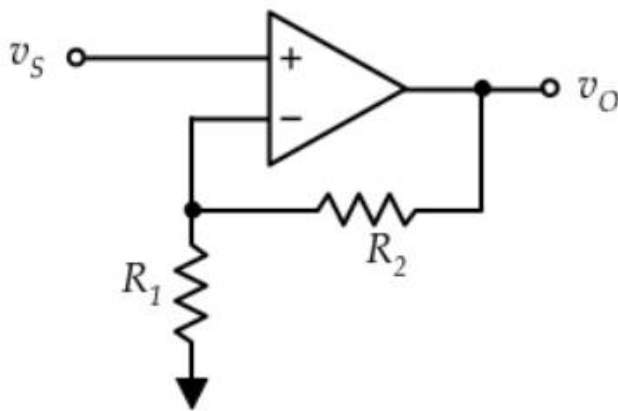Determine the closed-loop gain, $G = v_O / v_S$.




Answer

$$G = 23$$

In the circuit shown below $R_2 = 14 \text{ k}\Omega$.

Assume that the op-amp is ideal.

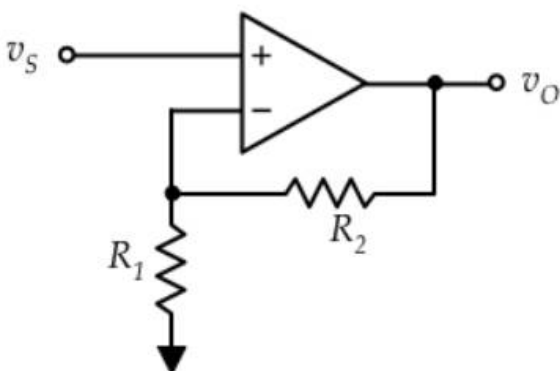Determine the value of R_1 so that the closed-loop gain, $G = v_O / v_S = 8$.




Answer

$$R_1 = 2 \text{ k}\Omega$$

In the circuit shown below $R_1 = 12\text{ k}\Omega$, $R_2 = 12\text{ k}\Omega$ and $R_3 = 72\text{ k}\Omega$

Assume that the op-amp is ideal.

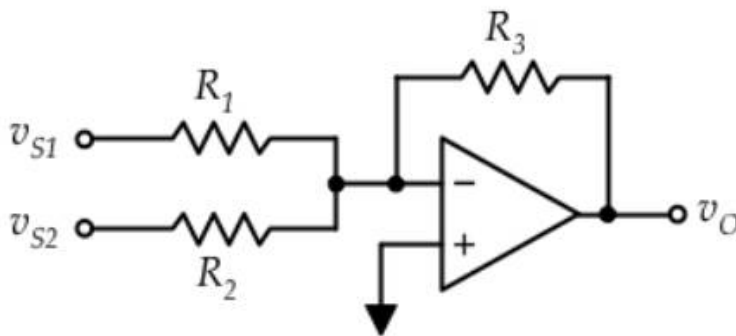If $v_{S1} = -0.4667\text{ V}_{\text{DC}}$ and $v_{S2} = 0.2\text{ V}_{\text{DC}}$ determine the DC output voltage.




Answer

$$v_O = 1.6\text{ V}_{\text{DC}}$$

In the circuit shown below $R_1 = 7.5\text{ k}\Omega$ and $R_2 = 112.5\text{ k}\Omega$.

Assume that the op-amp is ideal.

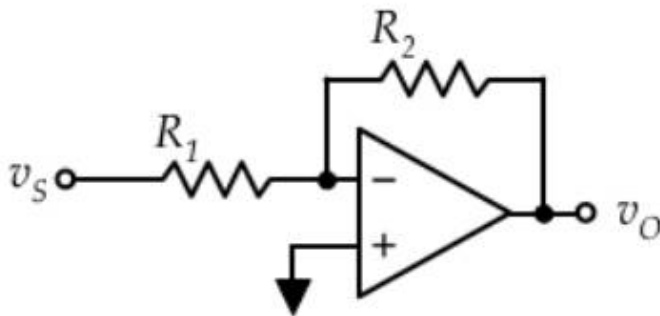Determine the closed-loop gain, $G = v_O / v_S$.




Answer

$$G = -15$$

In the circuit shown below $R_2 = 48 \text{ k}\Omega$.

Assume that the op-amp is ideal.

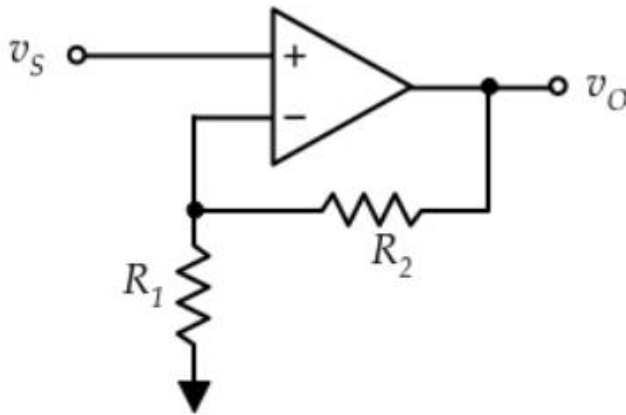Determine the value of R_1 so that the closed-loop gain, $G = v_O / v_S = 5$.




Answer

$$R_1 = 12 \text{ k}\Omega$$

In the circuit shown below $R_1 = 1 \text{ k}\Omega$ and $R_2 = 1 \text{ k}\Omega$.

Assume that the op-amp is ideal.

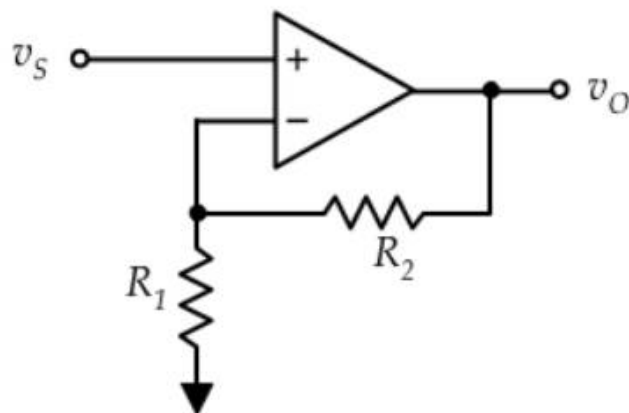Determine the closed-loop gain, $G = v_O / v_S$.




Answer

$$G = 2$$

In the circuit shown below $R_1 = 0.5 \text{ k}\Omega$.

Assume that the op-amp is ideal.

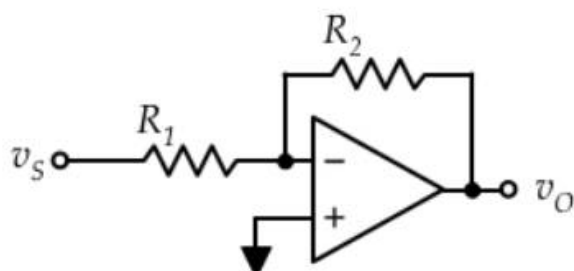Determine the value of R_2 so that the *magnitude* of closed-loop gain, $G = v_O / v_S$ is 17.




Answer

$$R_2 = 8.5 \text{ k}\Omega$$

In the circuit shown below $R_2 = 24 \text{ k}\Omega$.

Assume that the op-amp is ideal.

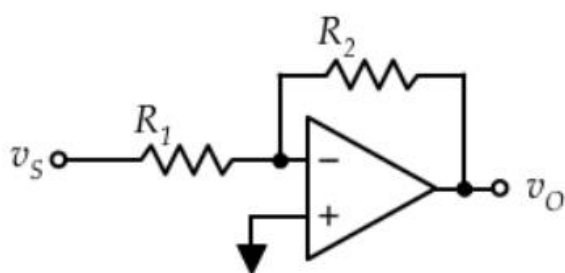Determine the value of R_1 so that the *magnitude* of closed-loop gain, $G = v_O / v_S$ is 24.



Answer

$$R_1 = 1 \text{ k}\Omega$$